

## Power in Circuits

$$P = \frac{\Delta U}{\Delta t}$$

Units: J/s or W

Power Supply:

$$P = IV$$

Resistors:

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$